

# Fully abstract categorical semantics for digital circuits

---

**George Kaye**, David Sprunger and Dan Ghica

University of Birmingham

20 July 2022

ACT 2022

## Joint work with...



David Sprunger



Dan Ghica

Digital circuits are everywhere!

How do we reason with them?

Generally by **simulation**

Reasoning in **software** is more **reduction-based**:


$$((\lambda x. \lambda y. x + y) 2) 5 =_{\beta} (\lambda y. 2 + y) 5 =_{\beta} 2 + 5 =_{\eta} 7$$

We want an **equational theory** for digital circuits

# Syntax

---

# Combinational circuit components

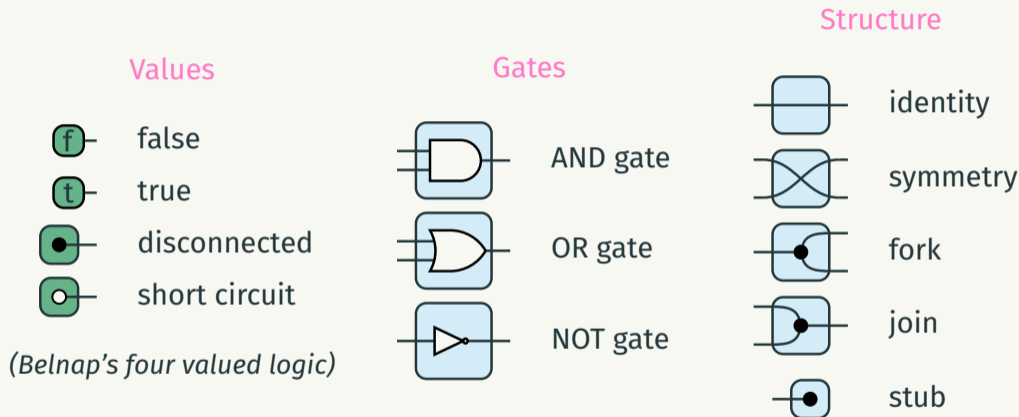


**Light** circuits  $\overset{m}{+} \boxed{F} \overset{n}{+}$  only contain gates and structure.

# Sequential circuit components

Delay




Feedback

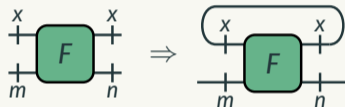

Dark circuits  $\overset{m}{+} \boxed{F} \overset{n}{+}$  may contain delay or feedback.

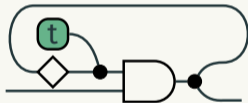Morphisms in a **freely generated symmetric traced monoidal category**







# Semantics


---
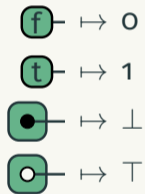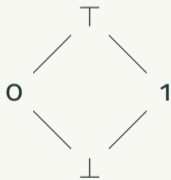
# Interpretation

Values are interpreted in a **lattice**  $\mathbf{V}$ :




# Interpretation

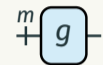

monotone functions
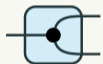
$$\bar{g}: \mathbf{V}^m \rightarrow \mathbf{V}$$



copy

$$x \mapsto (x, x)$$



join in the lattice

$$(x, y) \mapsto x \sqcup y$$



discard

$$x \mapsto \bullet$$

# Stream functions

The semantics of circuits is that of **stream functions**.

A **stream**  $\mathbf{V}^\omega$  is an infinite sequence of values.

A **stream function**  $f: (\mathbf{V}^m)^\omega \rightarrow (\mathbf{V}^n)^\omega$  consumes and produces streams.

# Causal stream functions

Not all stream functions correspond to sequential circuits...

**Causal**

Depends on past inputs

**Monotone**

with respect to the lattice

**'Finite'**

Specifies finite behaviours

## Theorem


*Every monotone causal stream function with 'finite behaviours' corresponds to a class of sequential circuits.*

## Equational reasoning

---
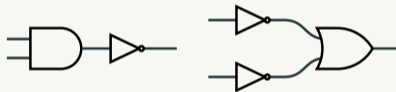
## Equality of circuits

When are two circuits equal? When they have the same **behaviour**



When they have the same **stream function**

Reasoning with streams is a **pain**.

# Productivity

We want to reason **equationally**: what equations do we need?


First goal: **productivity**.

A closed circuit is **productive** if it is equal to an **instant value** and a **delayed subcircuit** under the equational theory.






# Combinational equations

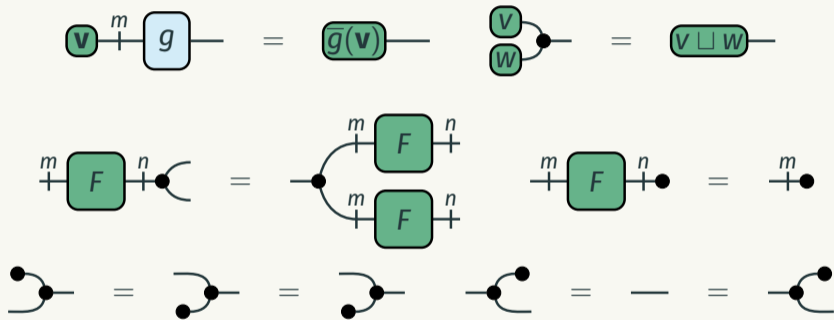

These reduce any closed combinational circuit  $v \xrightarrow{m} F \xrightarrow{n}$  to some  $w \xrightarrow{n}$ .

# Sequential equations

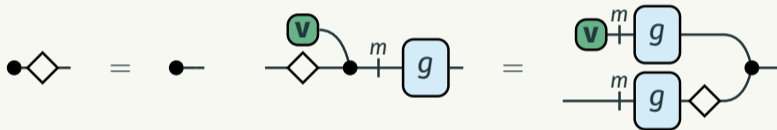

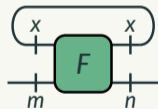
## Non delay-guarded feedback

How do we deal with something like this?




We need a way to eliminate non delay-guarded feedback.




## Non delay-guarded feedback

Our gates are **monotonic**, so they must have a **least fixed point**...  
Because the value set **V** is finite, we can always find this fixpoint!

# Non delay-guarded feedback

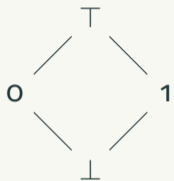

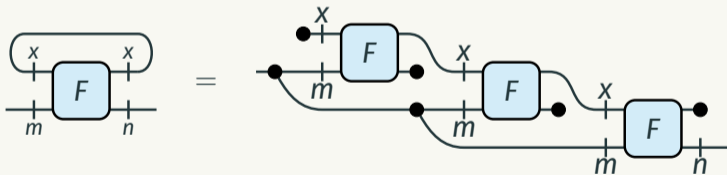
In  $\mathbf{V}$ , the length of the longest chain is 2...




We want




Axioms of STMCs

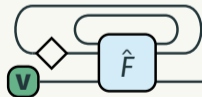


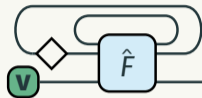




Eliminating 'instant feedback'

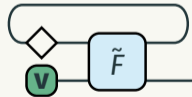






Axioms of STMCs

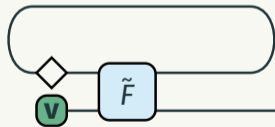
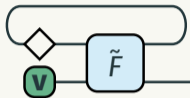


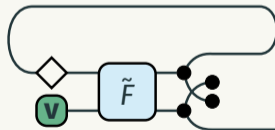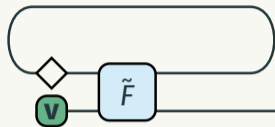


# Productivity

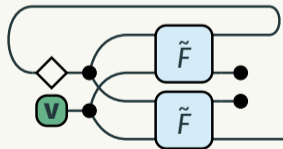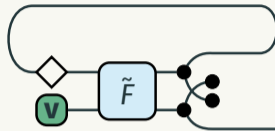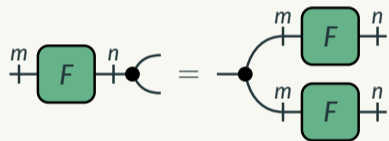


# Productivity

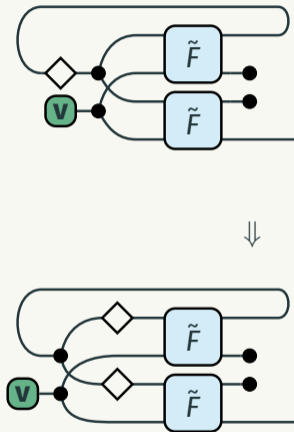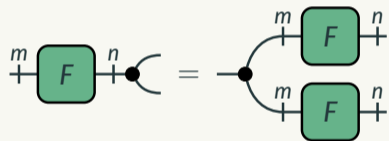



Axioms of STMCs

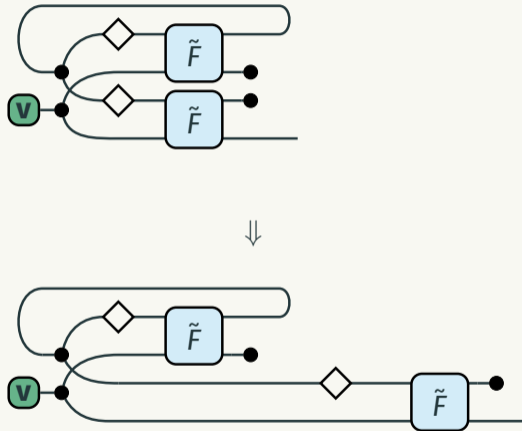



Axioms of STMCs

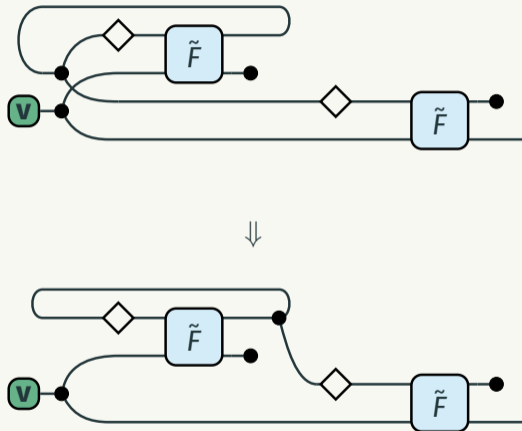

# Productivity


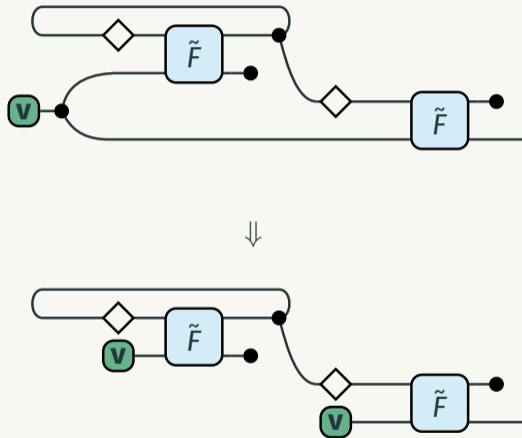
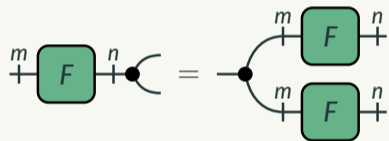


# Productivity

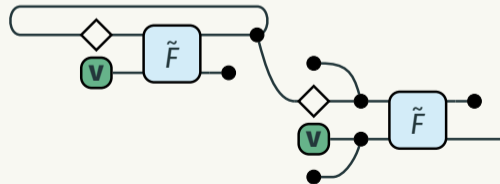
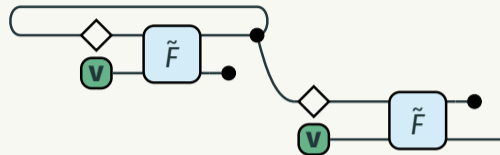





# Productivity

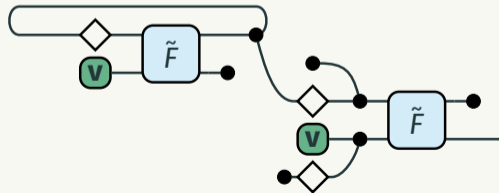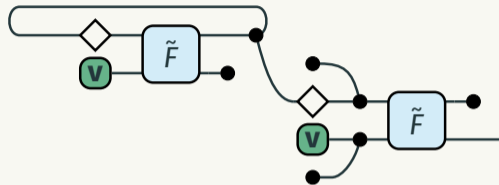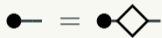


# Productivity

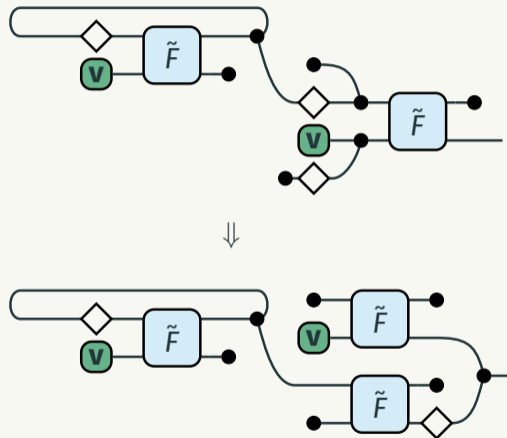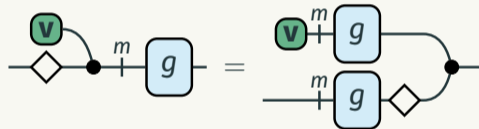


Combinational circuit equations

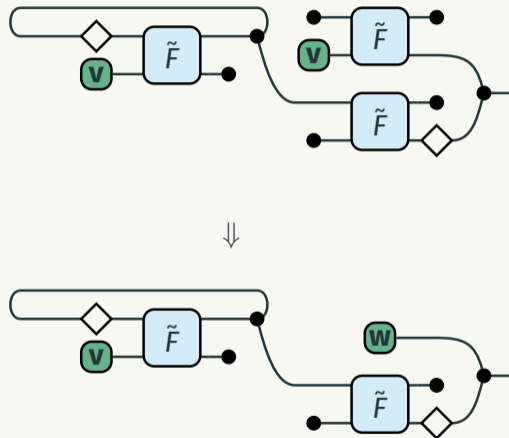

Tidying up

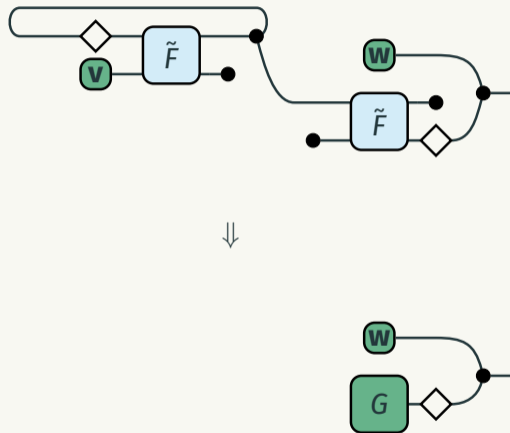

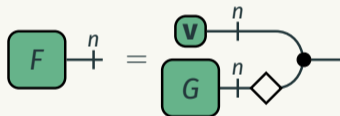
Any circuit has an **instantaneous value** and a **delayed subcircuit**.



These values are the elements of the corresponding stream!
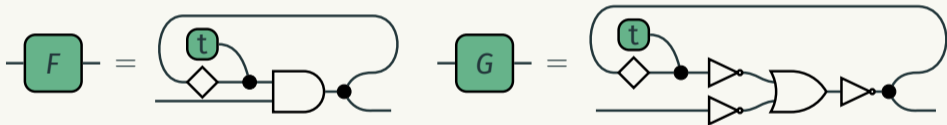
# Open circuits


We still cannot translate between **open** circuits with the same behaviour.



When do two circuits have the **same stream**?
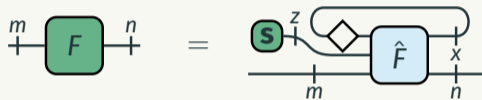
# Open circuits

We can think of circuits as **state machines**:



The circuit  produces the **state transition** and **output** of .

**Idea:** for all **accessible states**, if the **outputs** are equal then the **original circuits** are equal under the equational theory.

(cf. Mealy machine bisimulation)

## Theorem

$\overset{m}{+} \boxed{F} \overset{n}{+} = \overset{m}{+} \boxed{G} \overset{n}{+}$  if and only if their streams are equal.

## Proof.






## Theorem

$\overset{m}{+} \boxed{F} \overset{n}{+} = \overset{m}{+} \boxed{G} \overset{n}{+}$  if and only if their streams are equal.

## Proof.

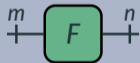

□

## Theorem

$\begin{matrix} m \\ + \end{matrix} \boxed{F} \begin{matrix} n \\ + \end{matrix} = \begin{matrix} m \\ + \end{matrix} \boxed{G} \begin{matrix} n \\ + \end{matrix}$  if and only if their streams are equal.

## Proof.




# Full abstraction

## Theorem

$\begin{matrix} m \\ + \end{matrix} \boxed{F} \begin{matrix} n \\ + \end{matrix} = \begin{matrix} m \\ + \end{matrix} \boxed{G} \begin{matrix} n \\ + \end{matrix}$  if and only if their streams are equal.

## Proof.

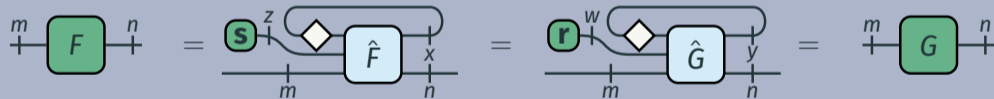

□

We have presented a **categorical framework** for sequential circuits

Circuits have semantics as **stream functions**

It is easier to reason **equationally**

We have **full abstraction**: a correspondence between syntactic and semantic

Next step: refine the **rewriting system**