

A compositional theory of digital circuits

George Kaye

University of Birmingham

07 February 2023 – LFCS seminar, Edinburgh

How we got here



'Hi Ohad, want to do a seminar at Birmingham?'


Six months later...

'How about you do a seminar at Edinburgh first?'




What are we going to be talking about?

Digital circuits!

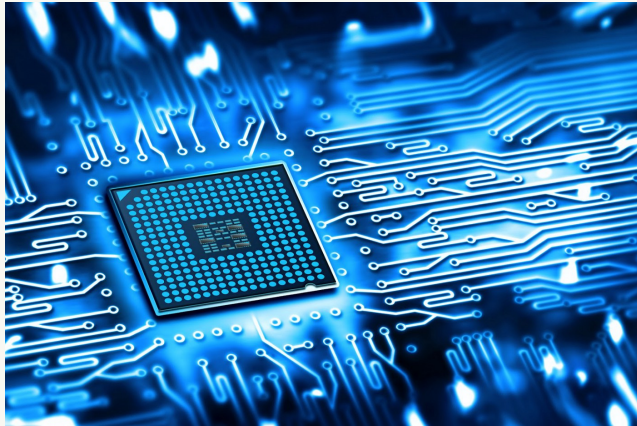


What are we going to be talking about?

Digital circuits!

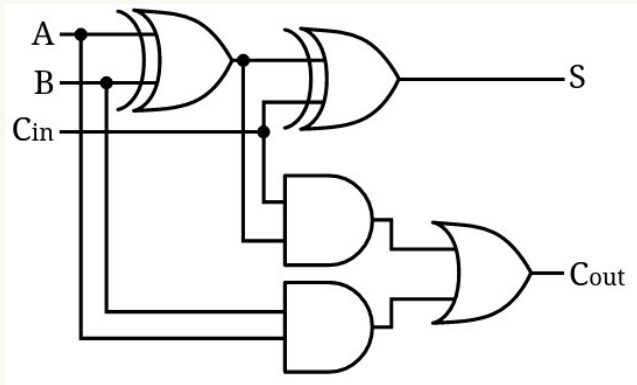

What are we going to be talking about?

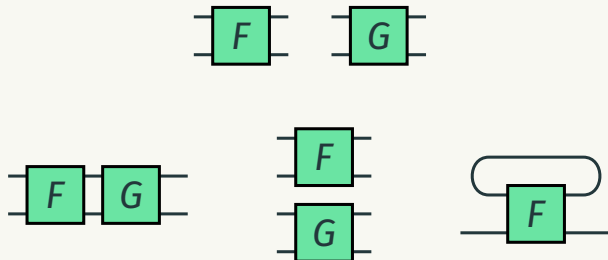We want a **compositional** theory of digital circuits.




These operations may look familiar to you!

Previous attempts foiled by **non-delay-guarded feedback**.


What came before

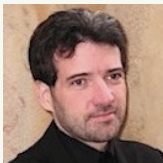Lafont (2003) *'Towards an algebraic theory of Boolean circuits'*



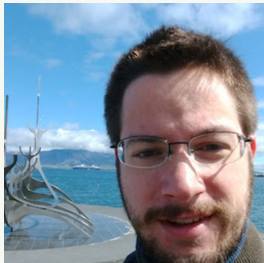Ghica, Jung, Lopez (2017) *'Diagrammatic semantics for digital circuits'*





David Sprunger
Indiana State University



Dan Ghica
University of Birmingham


(and me)



Syntax

Combinational circuit components

gates

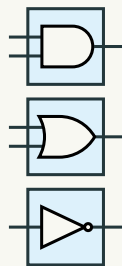


AND gate

OR gate

NOT gate

(co)monoid structure

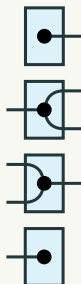

disconnected

fork

join


stub

categorical structure



identity

symmetry

Light circuits  only contain gates and structure.

Sequential circuit components

We need **state**.

Values




false



true



short circuit

Along with , models
*Belnap's four value
logic*

Delay




Feedback




\Rightarrow



Dark circuits  may contain delay or feedback.

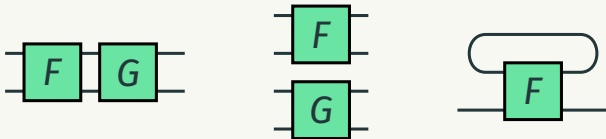Circuits are morphisms in a **freely generated symmetric traced monoidal category** (STMC).




SCirc

Semantics

We need some meaning

Values are interpreted in a **lattice**:

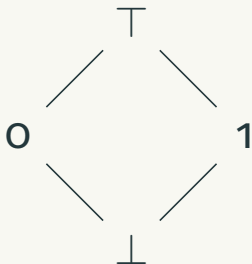

f $\mapsto 0$

t $\mapsto 1$

b $\mapsto \top$

• $\mapsto \perp$

Let's make everything a function



monotone functions

$$\bar{g}: \mathbf{V}^m \rightarrow \mathbf{V}$$



initialise

$$() \mapsto (\perp)$$



copy

$$x \mapsto (x, x)$$



join in the lattice

$$(x, y) \mapsto x \sqcup y$$



discard

$$x \mapsto \bullet$$

Feedback is interpreted as the **least fixed point**.

How do we model **delay**?

Streams!

A **stream** \mathbf{V}^ω is an infinite sequence of values.

$$V_0 :: V_1 :: V_2 :: V_3 :: V_4 :: V_5 :: V_6 :: V_7 :: \dots$$

A **stream function** $\mathbf{V}^\omega \rightarrow \mathbf{V}^\omega$ consumes and produces streams.

$$f(V_0 :: V_1 :: V_2 :: V_3 :: V_4 :: \dots) = W_0 :: W_1 :: W_2 :: W_3 :: W_4 :: \dots$$

Interpreting the sequential components

$$\boxed{V} - () := v :: \perp :: \perp :: \perp :: \dots$$

$$\boxed{\diamond} - (v_0 :: v_1 :: v_2 :: \dots) := \perp :: v_0 :: v_1 :: v_2 :: \dots$$

Does every circuit correspond to a stream function

$$(\mathbf{v}^m)^\omega \rightarrow (\mathbf{v}^n)^\omega?$$

No.

(but this is to be expected!)

Circuits are causal and monotone

Circuits are **causal**.

They can only depend **what they've seen so far**.

Circuits are **monotone**.

They are constructed from **monotone functions**.

Is that all? **Not quite...** (but we'll get there)

Some operations on stream function

Given a causal stream function $f: (\mathbf{V}^m)^\omega \rightarrow (\mathbf{V}^n)^\omega$ and an element $a \in \mathbf{V}^m$...


initial output $f[a] \in \mathbf{V}^n$

‘the first thing f produces given a ’

stream derivative $f_a \in (\mathbf{V}^m)^\omega \rightarrow (\mathbf{V}^n)^\omega$

‘how f behaves after seeing a first’

Hold on, these look familiar...

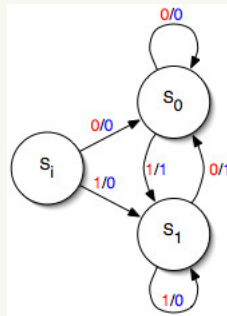

Mealy machine moment!

Stream functions are the *states* in a Mealy machine.

Circuits have finitely many behaviours

Circuits have a finite number of components.

So there are finite number of states in the Mealy machine.

So the outputs of streams given some input must be **periodic**.

(There are finitely many **stream derivatives**).

These are the streams we're looking for

Theorem

*A stream function is the interpretation of a sequential circuit if and only if it is **causal**, **monotone** and has **finitely many stream derivatives**.*

Equational reasoning

Now what?


We have a **sound and complete** semantics for circuits as **stream functions**.

But reasoning with streams can be a **pain**...


Why not reason **equationally**?

The two types of equation

Global

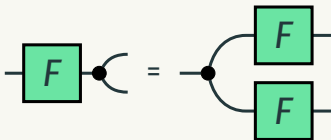

Local

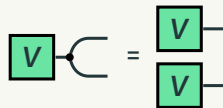

We want to stick to local equations as much as possible.

What do the values do?

Axiom(s)

$$\boxed{\bar{v}} \text{---} \boxed{g} \text{---} = \boxed{g(\bar{v})} \text{---}$$

$$\boxed{v} \text{---} \begin{array}{c} \text{---} \\ \text{---} \end{array} = \begin{array}{c} \boxed{v} \text{---} \\ \boxed{v} \text{---} \end{array}$$

$$\bullet \text{---} \diamond \text{---} = \bullet \text{---}$$

$$\begin{array}{c} \boxed{v} \\ \boxed{w} \end{array} \text{---} \bullet \text{---} = \boxed{v \sqcup w} \text{---}$$


$$\boxed{v} \text{---} \bullet = \boxed{}$$


For $\boxed{\bar{v}}$ and $\text{---} \boxed{F}$, there exists $\boxed{\bar{w}}$ such that $\boxed{\bar{v}} \text{---} \boxed{F} \text{---} = \boxed{\bar{w}}$.

Let's get structural

(, , , ,) is a **bialgebra**.


Axiom(s)

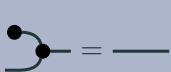

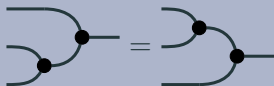






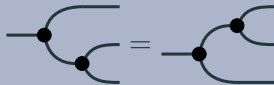



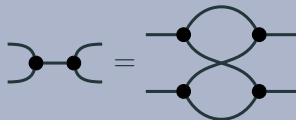








Splitting things up

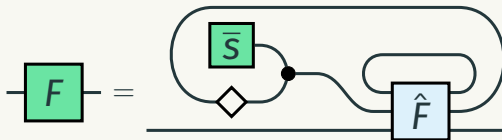Isolate the sequential and combinational components...



This is *almost* another Mealy machine moment...




...but there is the non-delay-guarded trace!

Do we even need it?

In industry, normally circuits must be **delay-guarded**.

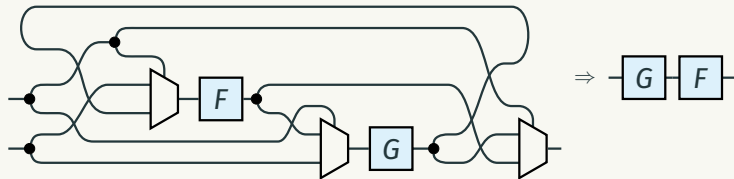But this rules out some **clever** circuits!




(And also it would be cheating)

Getting rid of non-delay-guarded feedback

V is a **finite** lattice...

The functions are monotone...

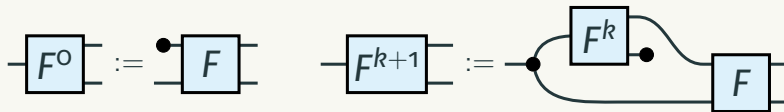
We can compute the **least fixed point** in finite iterations!



Axiom(s)




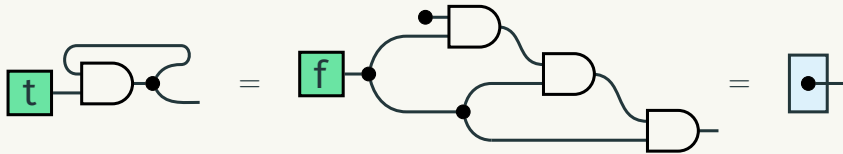Getting rid of non-delay-guarded feedback



Here's Mealy

For **any** circuit


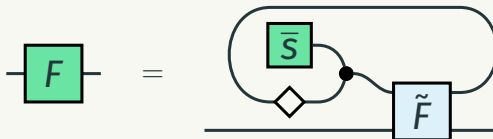


Let's get (even more) structural

What more structure can we add?

Forking is natural...


Axiom(s)

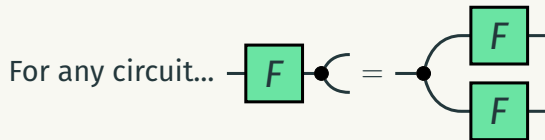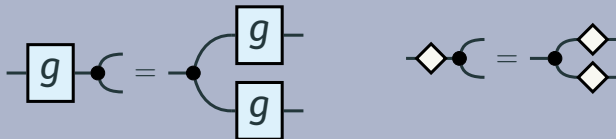


Let's (even even more) structural


Let's do the same for **stubbing**...

Axiom(s)

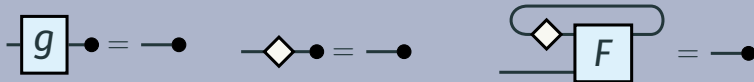


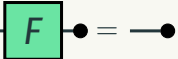For any circuit... 


Let's get structural

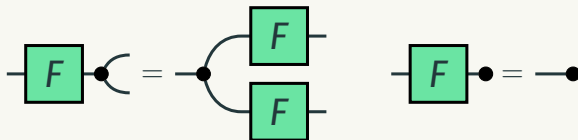

Cartesian!


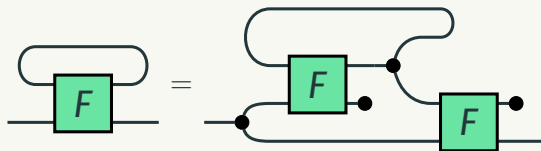


Goal:

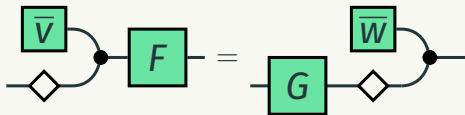


Running the simulation

Axiom(s)

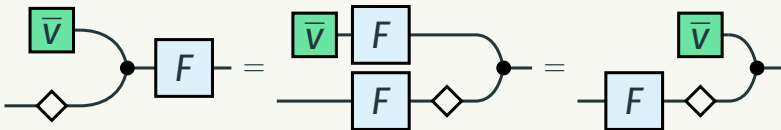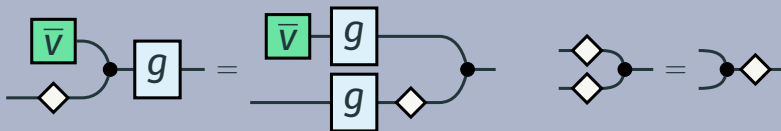


Running the simulation

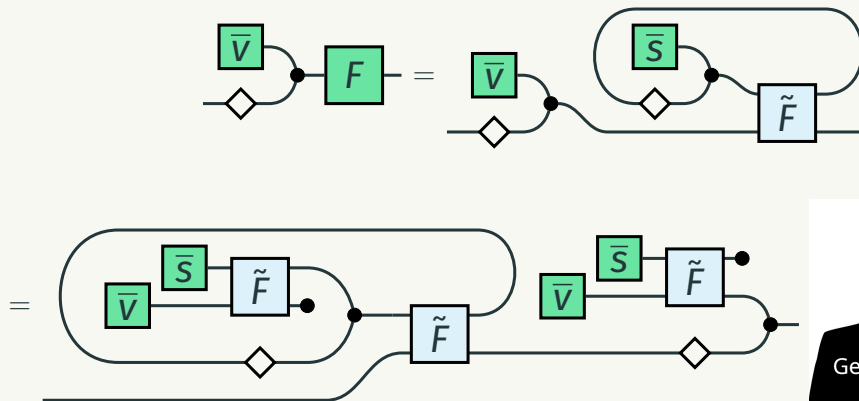

We made it!

We have defined a **sound and complete** compositional theory of digital circuits.

Also defined an **equational theory** for sequential circuits!

 Ghica, Dan R., K., and David Sprunger (2022). *A compositional theory of digital circuits*. URL: <https://arxiv.org/abs/2201.10456>.

(currently not the most up to date version...)